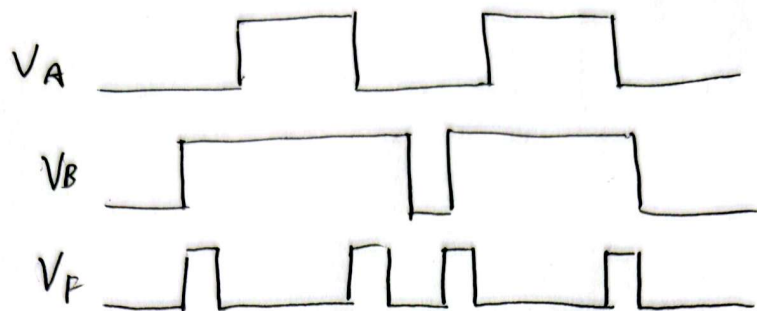


7-3. $V_B = 0V$ 时, $V_O = V_F = 0V$.
 $V_B = 5V$ 时, 构成施密特触发器的非门.



7-11. $q = \frac{R_1}{R_1 + R_2} = \frac{1}{4}$, $\Rightarrow R_2 = 3R_1$

$f = 20kHz = 2 \times 10^4 Hz$,

$T = \frac{1}{f} = 5 \times 10^{-5} s$.

取 $C = 0.1 \mu F$, 由 $T = 0.7(R_1 + R_2)C$ 可得

$R_1 = 180 \Omega$, $R_2 = 540 \Omega$

7-15

(1) 每个 555 定时器各自构成一个多谐振荡器

