
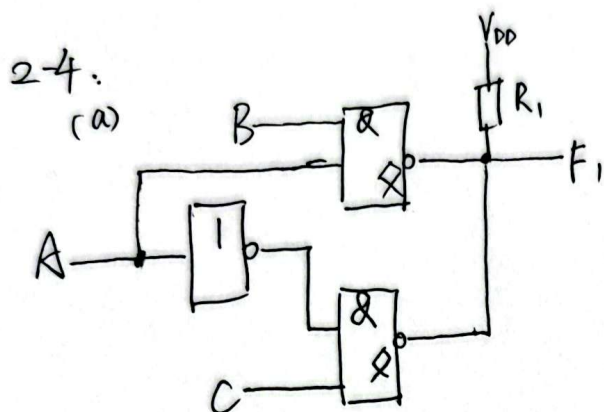


2-1: 对与非门影响: 对与非门本身无影响


对前级影响: 将使前级拉电流负载随并联输入端数目成正比增加

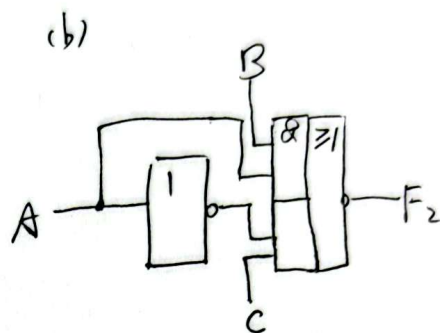

$$F_1 = \overline{(\overline{A}B)} \cdot \overline{(\overline{A}C)}$$


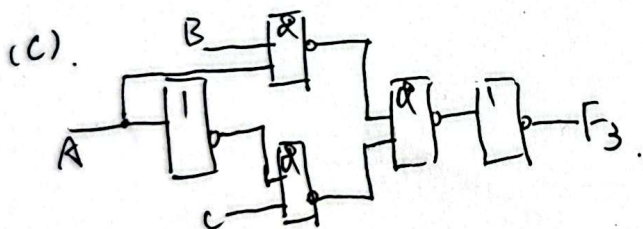
$$F_2 = \overline{(\overline{A}B + \overline{A}C)} \\ = \overline{A}B \cdot \overline{A}C$$



$$F_3 = \overline{(\overline{A}B \cdot \overline{A}C)} = \overline{A}B \cdot \overline{A}C$$

$F_1 = F_2 = F_3$, 功能一样.

2-12. (a)

2-6.

(1) $F_1 = \overline{A} + C$

(2) $F_2 = AB$

(3) $F_3 = A$

$$(\overline{ABE})(\overline{CDE}) \\ = \overline{ABE} \cdot \overline{CDE}$$

